


Program	B.Tech (CSE +ME+CE+EE) (C1 group)	Semester: 1
Subject Code	BTAM-101-23	Subject Title: Engineering Mathematics-I

ASSIGNMENT


Q No.	Questions
1.	Test the convergence or divergence of $x^2 + \frac{2^2}{3.4} x^4 + \frac{2^2 \cdot 4^2}{3.4.5.6} x^6 + \frac{2^2 \cdot 4^2 \cdot 6^2}{3.4.5.6.7.8} x^8 + \dots$
2.	State Cauchy Integral test. Use it to prove p-test for the convergence and divergence of the series $\sum_{n=1}^{\infty} \frac{1}{n^p}$; $p>0$.
3.	Test the convergence or divergence of the series: $\sum_{n=1}^{\infty} (-1)^{n-1} \frac{n}{2n-1}$.
4.	Discuss the nature of the series: $\frac{1}{2} + \frac{2}{3} x + \left(\frac{3}{4}\right)^2 x^2 + \left(\frac{4}{5}\right)^3 x^3 + \dots$, for $x > 0$.
5.	Show that the sequence $\{\frac{2n-7}{3n+2}\}$ is monotonic increasing. Also check if it is convergent or not?
6.	Test the convergence of the sequence: a) $s_n = 2 + (-1)^n$, b) $s_n = \{\frac{2n^3+7n}{5n^3+3n^2}\}$.
7.	Test the convergence of the series: $\frac{1}{1.2.3} + \frac{3}{2.3.4} + \frac{5}{3.4.6} + \dots$
8.	Test the convergence or divergence of $\frac{x}{1.2} + \frac{x^2}{2.3} + \frac{x^3}{3.4} + \dots, x > 0.$
9.	Test the convergence or divergence of $1 + \frac{2x}{2!} + \frac{3^2 x^2}{3!} + \frac{4^3 x^3}{4!} + \dots, x > 0.$
10.	Test the convergence or divergence of $\frac{x}{1} + \frac{1}{2} \frac{x^3}{3} + \frac{(1.3)}{2.4} \frac{x^5}{5} + \frac{1.3.5}{2.4.6} \frac{x^7}{7} + \dots, x > 0.$

29/01/24

RLC circuits

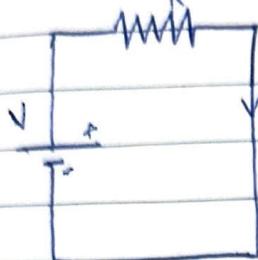

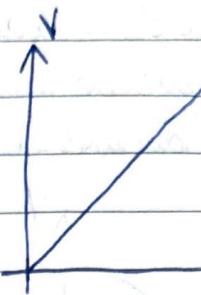I \downarrow Ohm's law \rightarrow
to determine the relationship
between voltage & current.



$$V = IR \quad \left\{ \begin{array}{l} \text{when all physical conditions} \\ \text{like temperature remain constant.} \end{array} \right.$$

$$R = \frac{V}{I}$$

- B Why battery discharges when not in use?
→ because of internal resistance in battery.

Commercial Unit of
Energy = kWh


$$P = VI$$

(Watt)

- B 2 Fans of rating 80W works 10 hrs daily.
4 LEDs of rating 20W works 12 hrs daily.
1 AC of rating 1.5 KW works 10 hrs daily.
1 Geyser of rating 3kW works 1 hr daily.
1 60W charger works 3 hrs daily.
Calculate units consumed per day.

$$\begin{aligned} & \rightarrow \frac{2 \times 80 \times 10}{1000} + \frac{4 \times 20 \times 12}{1000} + \frac{1 \times 1.5 \times 10}{1000} + \frac{1 \times 3 \times 1}{1000} + \frac{1 \times 60 \times 3}{1000} \\ &= 1.6 + 0.96 + 15 + 3 + 0.18 \\ &= \boxed{20.74 \text{ units Ans}} \end{aligned}$$


29/01/24

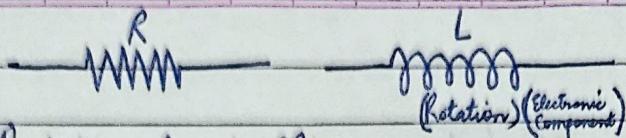

Resistive Load (R)

Capacitive Load (C)


Inductive Load (L)

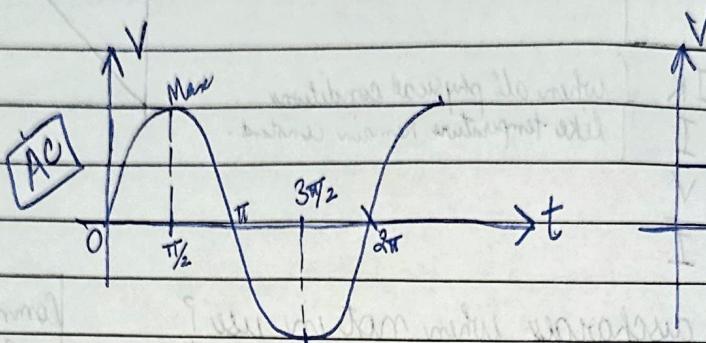

Kirchoff's Laws :-


- ① KCL ($\sum i = 0$)
- ② KVL ($\sum V = 0$)

KCL

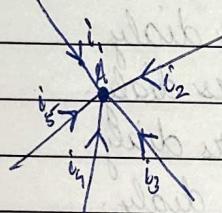

at A


$$i_1 + i_2 + i_3 + i_4 + i_5 = 0$$

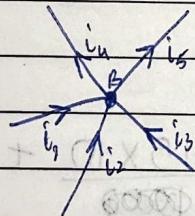

at B


$$i_1 + i_2 + i_3 = i_4 + i_5$$

KCL

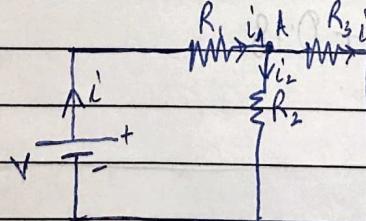


KCL at A

$$i_1 = i_2 + i_3$$

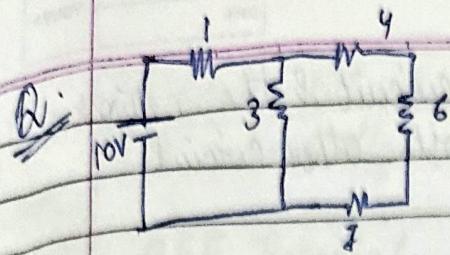

$$R_{eq} = \frac{17 \times 3 + 20}{20} = \frac{71}{20}$$
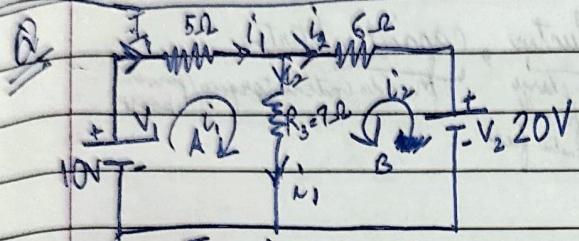
$$i = \frac{10 \times 20}{71} = \frac{200}{71} \text{ A} \quad \underline{\text{Ans}}$$



$$I = i_1 + i_2 \quad (\text{KCL})$$

$$\text{around A: } 10 - i_1 \times 5 - 7 \times (i_2 + i) = 0 \quad (\text{KVL}) \Rightarrow$$

$$\text{around B: } 20 - 6 i_2 - 7(i_2 + i) = 0 \quad \Rightarrow$$



30/01/24

Electrical Network → no loop

not connected

Combo of various electric elements (L, C, R), voltage source, current source

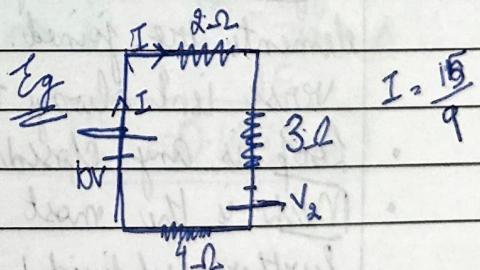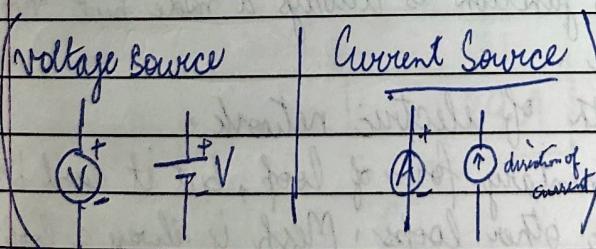Types :- ① Passive Elements ② Active Elements



$$I = \frac{15}{9}$$

$$\text{KVL: } 15 - \frac{15}{9} \times 2 - \frac{15}{9} \times 3 - \frac{15}{9} \times 4 = 0$$

Active Elements supply energy to the circuit & the network containing these sources together with other circuit elements.

~~Old Regulator~~ Resistance based
Same power on all ~~speeds~~ for speeds.

Passive Elements receive energy/absorb energy and then either convert it into heat or store it in an electric/magnetic field is called Passive Elements.

Eg Resistor, transformer, inductor, capacitor/starter

pure charge provides initial torque/power boost
in form of magnetic field

Bilateral & Unilateral Elements

If by reversing the terminal connections of element in circuit, the circuit response remains same: Eg L, C, R


If by reversing the terminal connections of an element in a circuit, the circuit response gets changed. Eg Voltage Source, Diode, Current Source

- A Node of a Network is an equipotential surface at which two or more circuit elements are joined.
- A Junction is that point in an electric circuit where three/more elements are joined. So, junction is always a node but vice-versa isn't always true.
- Loop is any closed path of electric network.
- Mesh is the most elementary form of loop, but it can't be further subdivided into other loops. Mesh is always a loop, but vice-versa isn't always true.
- Lumped Network is a network in which physically separate resistors, capacitors and inductors can be represented.

Distributed Network in which R, L, C can't be physically separated and individually isolated as separate elements. Eg. Transmission line

31/01/24

BEE Tutorial

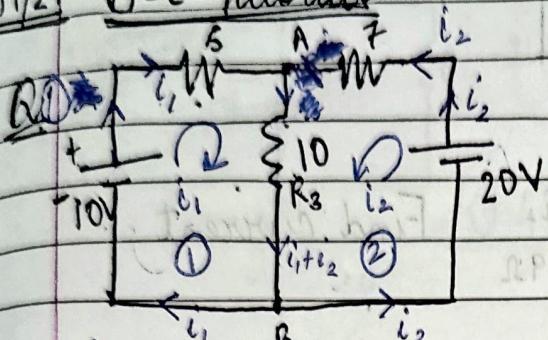

Find current across R_3

~~$i_{l3} = \frac{20 - 10}{R_3} = 1A$~~

in loop ①

$$10 - 5i_1 - 10(i_1 + i_2) = 0$$

$$10 = 15i_1 + 10i_2 \Rightarrow \frac{10 - 10i_2}{15} = i_1$$

in loop ②

$$20 - 7i_2 - 10(i_1 + i_2) = 0$$

$$20 = 17i_2 + 10i_1$$

$$0 = 10 - 20 = 17i_2 + 10\left(\frac{10 - 10i_2}{15}\right)$$

$$60 = 51i_2 + 20 - 20i_2$$

$$40 = 31i_2$$


$$i_2 = \frac{40}{31} A \Rightarrow i_1 = 10 - \frac{400}{31} \cdot \frac{15}{10} A$$

$$i_2 = 1.29 A$$


$$i_1 = -0.1935 A$$

Current across $R_3 = i_1 + i_2$

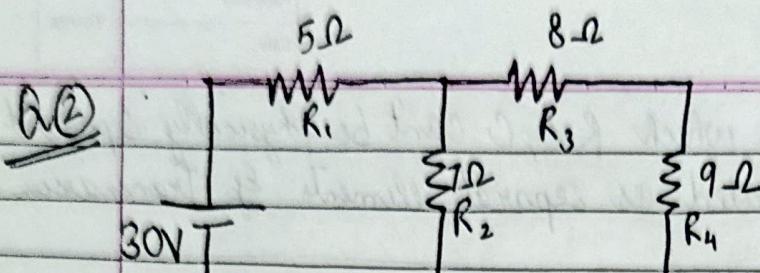~~(1) $\Rightarrow 1.0965 A$ Ans
(2) $i = 1.0965 A$~~



Find current flowing in the circuit.

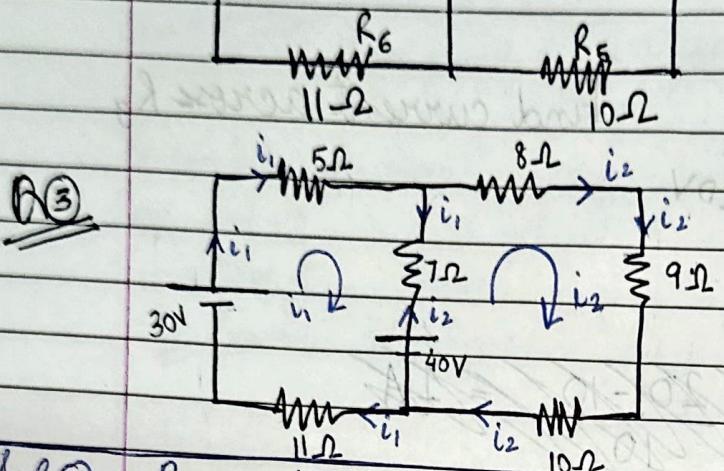

Find current.

Sol(2) $R_{eq} = \frac{(9+8+10) \times 7}{9+8+10+7} + 5 + 11$

$$R_{eq} = \frac{27 \times 7}{34} + 5 + 11 = 21.558\Omega$$

$$i = \frac{V}{R_{eq}} = \frac{30}{21.558} = 1.391\text{ A} \quad \boxed{\text{Ans}}$$

Sol(3)

loop 1

$$30 - 5i_1 - 11i_1 - 40 - 7(i_1 - i_2) = 0$$

$$30 - 40 = 23i_1 + 7i_2$$

$$-10 = 23i_1 + 7i_2 \Rightarrow -10 - 23i_1 = i_2 \quad 7$$

loop 2

$$40 - 7(i_2 - i_1) - 8i_2 - 9i_2 - 10i_2 = 0$$

$$40 = -7i_1 + 34i_2$$

$$40 = -7i_1 + 34 \left(\frac{-10 - 23i_1}{7} \right)$$

$$280 = -49i_1 - 340 - 782$$


$$49i_1 = -1402$$

$$i_1 = -28.61\text{ A}$$

$$i_2 = -10 - 23(-28.61) = 692.58\text{ A}$$

$$\text{Current} = i_1 + i_2 = 121.19 \text{ A}$$

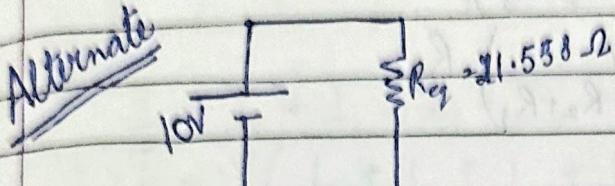\therefore Current in Circuit = 121.19 A [Ans]



$$i = \frac{10}{21.558} = 0.463 \text{ A}$$

5/02/24 Current Division Rule :-

$$I_1 = \frac{V_1}{R_1}, I_2 = \frac{V_1}{R_2}$$


$$I = I_1 + I_2 \quad \because (\text{KCL})$$

$$I = \frac{V_1}{R_1} + \frac{V_1}{R_2} = V_1 \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$


$$V_1 = I \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$I_1 = \frac{V_1}{R_1} = \frac{I}{R_1} \left(\frac{R_1 R_2}{R_1 + R_2} \right) = I \left(\frac{R_2}{R_1 + R_2} \right)$$
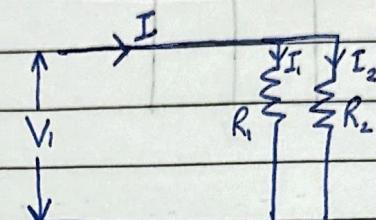
$$I_2 = \frac{V_1}{R_2} = \frac{I}{R_2} \left(\frac{R_1 R_2}{R_1 + R_2} \right) = I \left(\frac{R_1}{R_1 + R_2} \right)$$



Voltage Division Rule :-

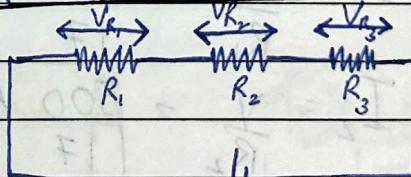

$$V_{R_1} = IR_1 \quad \text{--- (1)}$$

$$V_{R_2} = IR_2 \quad \text{--- (2)}$$

$$V_{R_3} = IR_3 \quad \text{--- (3)}$$

$$V = V_{R_1} + V_{R_2} + V_{R_3} \quad \because (\text{KVL})$$

~~$$V = V_{R_1} + V_{R_2} + V_{R_3}$$~~

$$V = IR_1 + IR_2 + IR_3$$

$$V = I(R_1 + R_2 + R_3)$$


$$I = \frac{V}{R_1 + R_2 + R_3}$$

$$V_{R_1} = I \times R_1 = \left(\frac{V}{R_1 + R_2 + R_3} \right) R_1$$

$$V_{R_2} = I \times R_2 = \left(\frac{V}{R_1 + R_2 + R_3} \right) R_2$$

$$V_{R_3} = I \times R_3 = \left(\frac{V}{R_1 + R_2 + R_3} \right) R_3$$

Ques)

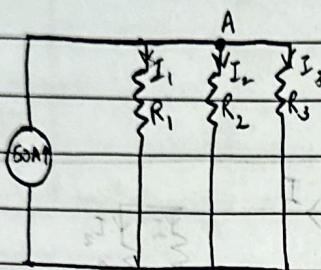

Find current in all resistance
using KCL.

$$\begin{aligned} R_1 &= 2\Omega \\ R_2 &= 1\Omega \\ R_3 &= 5\Omega \end{aligned}$$

$$50 = I_1 + I_2 + I_3$$

$$50 = V_A \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = V_A \left(\frac{1}{2} + \frac{1}{1} + \frac{1}{5} \right) = V_A \left(\frac{5+10+2}{10} \right)$$

$$50 = V_A \left(\frac{17}{10} \right)$$

(p.d) $V_A = \frac{500}{17} V$


$$I_1 = \frac{V}{R_1} = \frac{500}{17} \times \frac{1}{2} = \frac{250}{17} A = I_1 \quad \text{Ans}$$

$$I_2 = \frac{V}{R_2} = \frac{500}{17} A = I_2 \quad \text{Ans}$$

$$I_3 = \frac{V}{R_3} = \frac{500}{17} \times \frac{1}{5} = \frac{100}{17} A = I_3 \quad \text{Ans}$$

* Ground Potential = 0

(Ques)

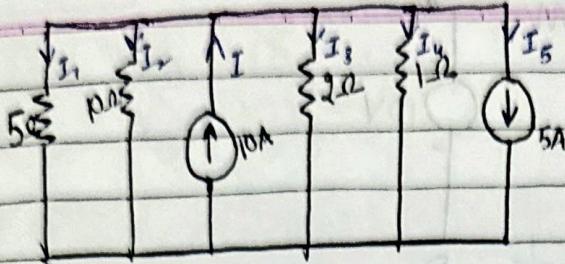

$$\rightarrow I = I_1 + I_2 + I_3 + I_4 + I_5$$

$$I - I_3 = V_A \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$5A = V_A \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{2} + \frac{1}{1} \right) = V_A \left(\frac{20+10+50+100}{100} \right)$$

$$5 = V_A \left(\frac{180}{100} \right)$$

$$\boxed{\frac{50V}{18} = V_A}$$

$$I_1 = \frac{V_1}{R_1} = \frac{50}{18} \times \frac{1}{5} = \frac{10}{18} A = I_1 \text{ Ans}$$




$$I_2 = \frac{V_1}{R_2} = \frac{50}{18} \times \frac{1}{10} = \frac{5}{18} A = I_2 \text{ Ans}$$

$$I_3 = \frac{V_1}{R_3} = \frac{50}{18} \times \frac{1}{2} = \frac{25}{18} A = I_3 \text{ Ans}$$


$$I_4 = \frac{V_1}{R_4} = \frac{50}{18} \times \frac{1}{1} = \frac{50}{18} A = I_4 \text{ Ans}$$

5/02/24


(Ques)

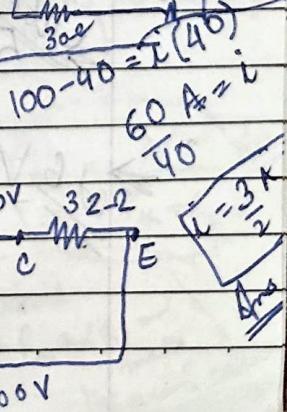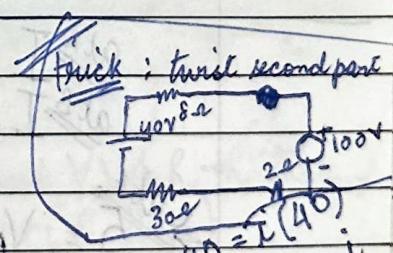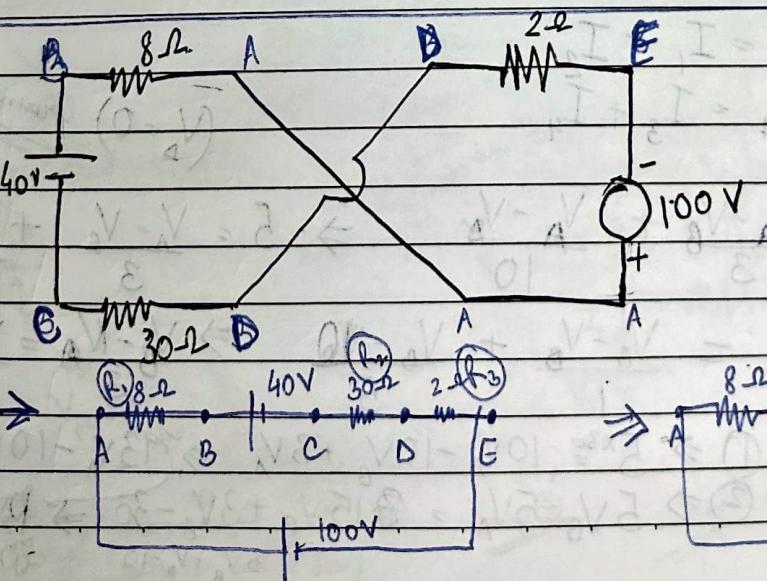

(Ans)

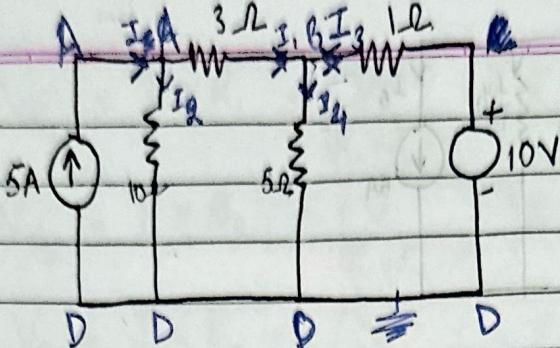
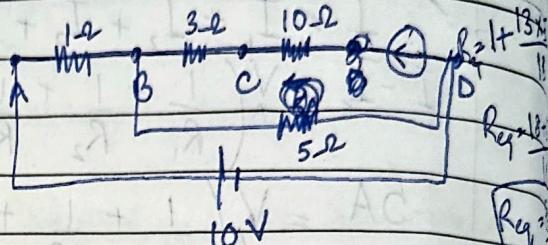
$$\begin{aligned} I &= I_1 + I_2 \\ I &= I_3 + I_4 \end{aligned}$$



$$I = \frac{180}{83} A$$

$$I = \frac{10}{10+3+1} = \frac{10}{14} A$$

$$V_{AB} = \frac{180}{83} V$$

$$I = \frac{10 \times 18}{83} = \frac{180}{83}$$

$$V_{BD} = 10 - \frac{180}{83} = \frac{650}{83} V$$

$$I_{5\Omega} = \frac{130}{83} A$$

$$\frac{130}{83 \times 5}$$

$$\begin{aligned} I &= I_1 + I_2 \\ I_1 &= I_3 + I_4 \\ I &= I_3 + I_4 + I_2 \\ I &= -5 + 130 \end{aligned}$$

$$\begin{aligned} \text{at } A \quad I &= I_1 + I_2 \\ \text{at } B \quad I_1 &= I_3 + I_4 \end{aligned}$$

(V_A = 0) ground potential

$$\Rightarrow 5 = \frac{V_A - V_B}{3} + \frac{V_A - V_B}{10} \Rightarrow 5 = \frac{V_A - V_B}{3} + \frac{V_A - V_B}{10}$$

$$\Rightarrow \frac{V_A - V_B}{3} = \frac{V_B - V_A}{1} + \frac{V_B - V_A}{5} \Rightarrow V_B - V_A = \frac{V_B + V_A}{5}$$

$$\begin{aligned} ① \Rightarrow 5 &= 10V_A - 10V_B + 3V_A \Rightarrow 13V_A - 10V_B = 150 \\ ② \Rightarrow 5V_B - 5V_A &= 3V_B + 3V_A - 30 \Rightarrow 2V_B - 10V_A = 30 \end{aligned}$$

$$5V_B + V_A - 10 = 30$$

~~$10V_A - V_B = 15$~~

~~$V_B = 10V_A - 15$~~

~~$-13V_B - 5V_A = -30$~~

~~$5V_A + 13V_B = 30$~~

~~$V_A = \frac{30 - 13V_B}{5}$~~

~~$③ \Rightarrow 13V_A - 10(10V_A - 15) = 150$~~

~~$13V_A - 100V_A + 150 = 150$~~

~~$③ \Rightarrow 13\left(\frac{30 - 13V_B}{5}\right) - 10V_A = 150$~~

$$V_A = 30 - 13\left(\frac{-360}{219}\right)$$

5

$$390 - 169V_B - 50V_B = 750$$

$$\boxed{V_A = 19.85V}$$

$$\boxed{V_B = 10.9V}$$



Ans

~~$219V_B = 360$~~

~~$\boxed{V_B = \frac{-360}{219}}$~~

6/02/24


Thevenin's Theorem :-

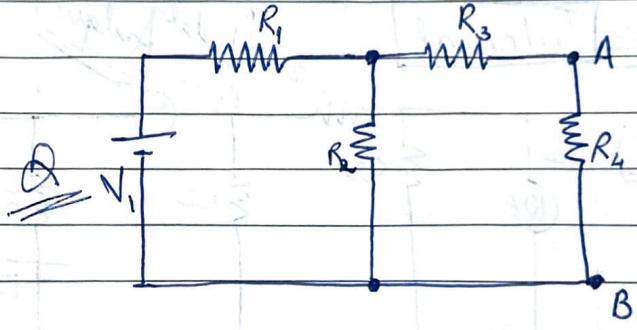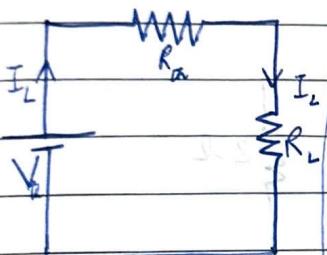

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


Find current across R_4 . (Find I_L)

Step ①

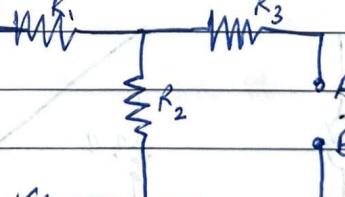

Step ②
Short voltage
make A+B points
(Remove R_4 and V_{th}) & $R_4 \rightarrow R_{th}$ (load resistance)

$$R_{th} = R_3 + (R_1 \parallel R_2)$$

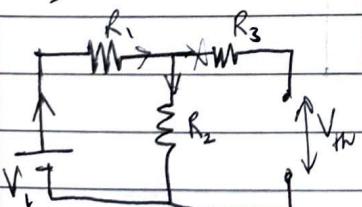


$$V_{th} = I_L \times R_2$$

$$V_{th} = R_2 \times \frac{V_1}{R_1 + (R_2 \parallel R_3)}$$

(no current will flow through R_3 as open circuit here)

Create a loop with V_1 and R_1 , R_2 , R_{th}


Step ③

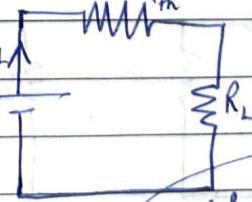


$$I_L = \frac{V_1}{R_{th} + R_L}$$

Replace whole circuit with R_{th} and R_L and make Thevenin's circuit

Ques)

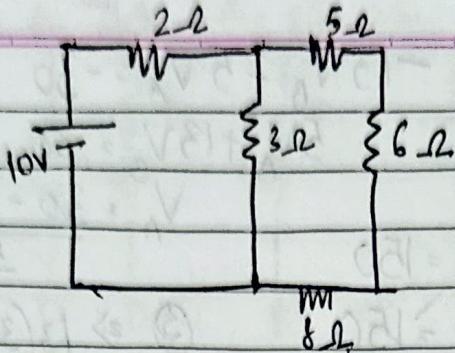

Ques)

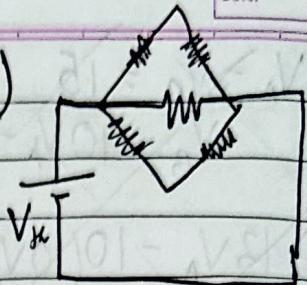

Steps :-


- ① Remove/open R_{AB} and name it as R_L .
- ② Short voltage (V)
- ③ Find R_{Th} across those two points A & B.
- ④ Replace whole circuit with R_{Th} , R_L and V and call it as Thévenin's Circuit.
- ⑤ Find I_L

7/02/24


Tutorial

Nodal Analysis


Q(1)

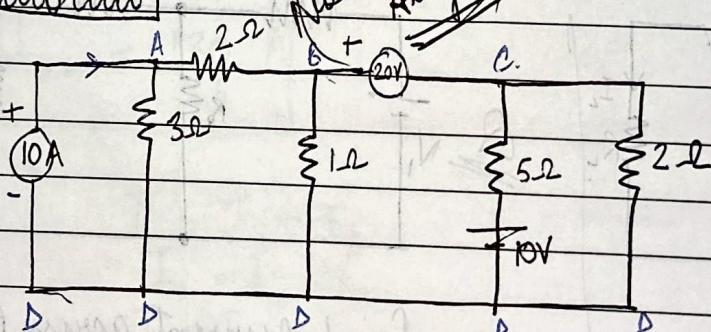

Q(2)

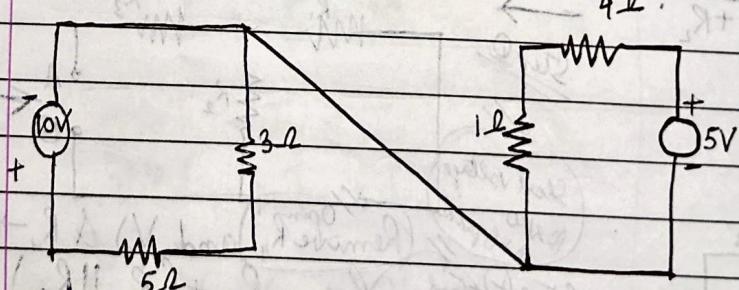

Q(3)
(Thévenin's
Theorem)

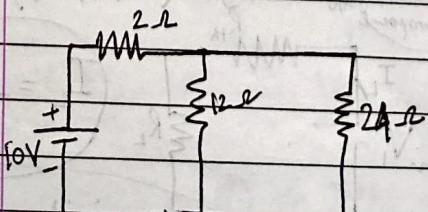


13/02/24

Granit Park

M	T	W	T	F	S	S
Page No.:						YOUVA
Date:						


Norton's Theorem :-

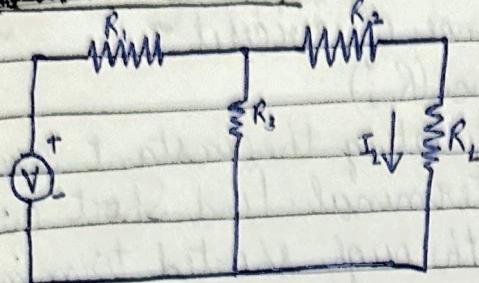

$$I = \frac{V}{(R_1 + R_2 + R_L)}$$

And short circuit (I_{sc})
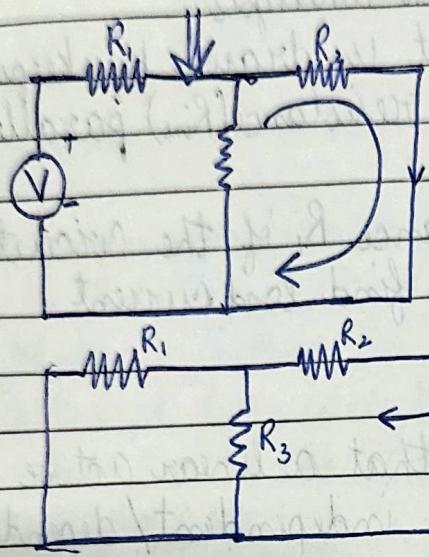
$$I_{sc} = I \left(\frac{R_3}{R_3 + R_2} \right)$$



$$R_{int} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$



Any two terminal linear network with current source, voltage source and resistance can be replaced by equivalent circuit consisting of a current source in parallel with resistance, the value of current source is the short circuit current between the two terminals of circuit and network of the resistance is the equivalent resistance measured between terminals of network with all the source replaced by their Internal Resistance.

I_L = Load Current

I_{sc} = Short Circuit Current

R_{int} = Internal Resistance of circuit

R_L = Load resistance

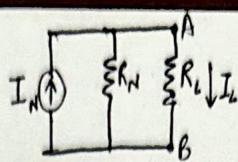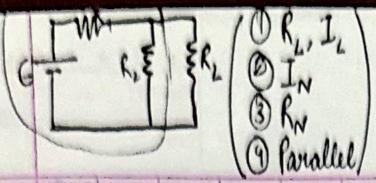

$$I_L = \frac{(\text{total current}) \times (\text{opposite branch resistance})}{(\text{total resistance})} = \frac{I_N}{R_L}$$



Notes:
Remove E
and remove load
make open in
both


Steps of Norton Theorem :-

- ① Remove the load resistance of circuit
- ② Find the internal resistance (R_{int})
- ③ Source Network by deactivating the constant source.
- ④ Now, short the load terminal. Find Short Circuit Current (I_{sc}) following through shorted terminal using conventional network analysis.
- ⑤ Norton equivalent circuit is drawn by keeping the ~~constant~~ internal resistance (R_{int}) parallel with I_{sc} .
- ⑥ Reconnect the load resistance R_L of the circuit across load terminal and find load current through it (I_L).


⇒ Norton's theorem states that a linear active network consisting of the independent/dependent voltage source/ current source. Various circuit elements can be substituted by eg. circuit consistency of the current source in parallel with resistance. The current source being I_{sc} across load terminal & resistance being R_{int} of the source network

Superposition Theorem :-

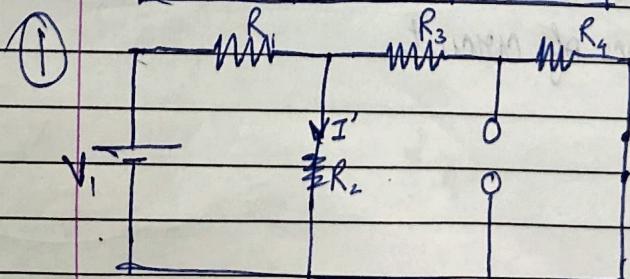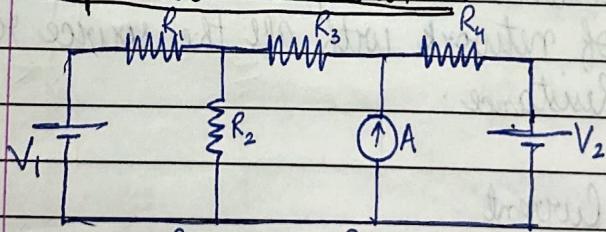

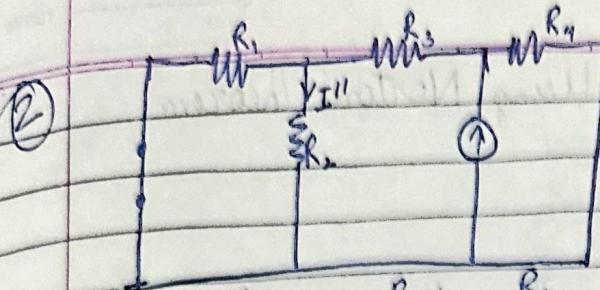

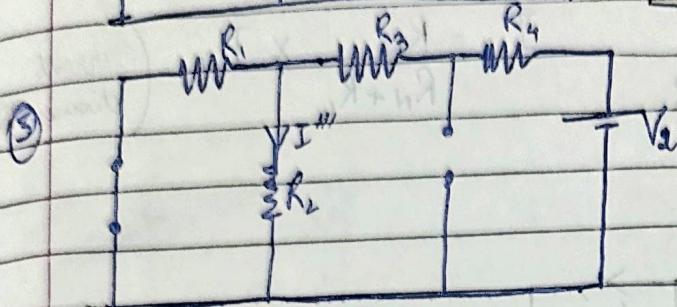
- If deactivate Voltage Source → Short Circuit
- If deactivate Current Source → Open Circuit




→ Superposition theorem states that in any linear, active bilateral network having more than one source, the response across any element is the sum of response obtained from each source, consider separately and all other sources are replaced.


Steps of Superposition Theorem :-

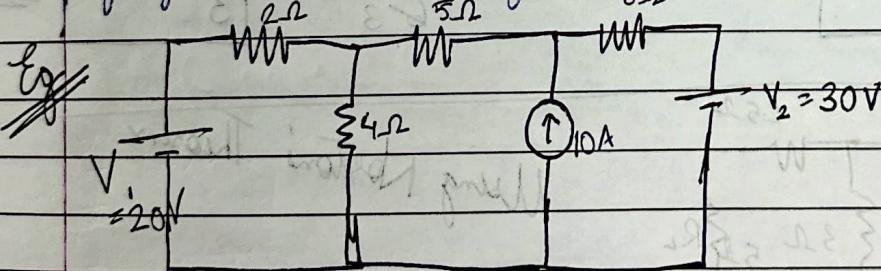- ① Take only one source voltage or current source and deactivate other sources.
- ② Find the current through the first source while if voltage source is shorted and current source is open.
- ③ If by active source, find the current I' , I'' , I''' , etc.




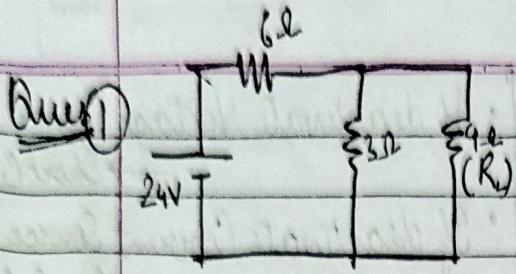


Using Norton's Theorem:

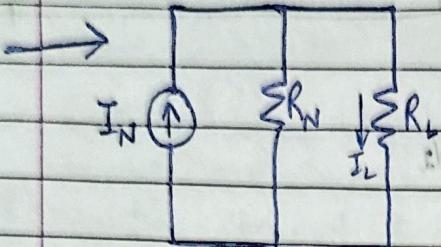

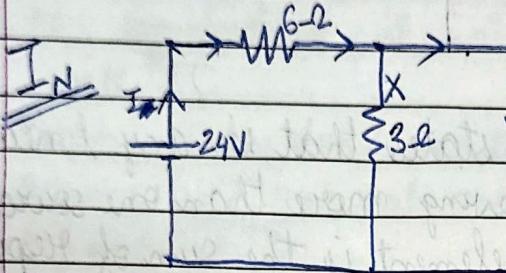
$$I_L = \frac{R_N}{R_N + R_L} \times I_N \quad (\text{Current division theory})$$



$$I_N = \frac{24}{6} = 4A$$

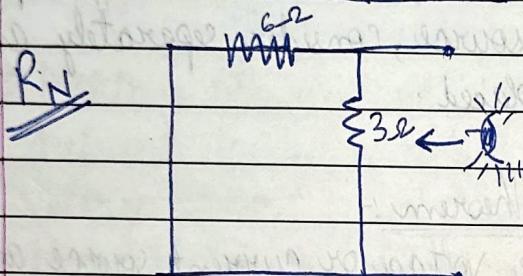

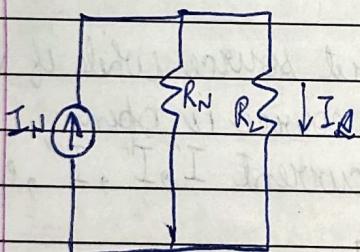
$$R_N = \frac{6 \times 3}{6 + 3} = \frac{6 \times 3}{9} = 2\Omega$$




$$I_L = \frac{R_N}{R_N + R_L} \times I_N = \frac{2}{2+4} \times 4$$

$$I_L = \frac{2 \times 4}{6} = \frac{4}{3} A = I_L$$

Ques 2

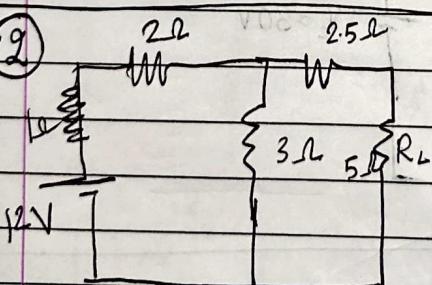

Using Norton's Theorem:

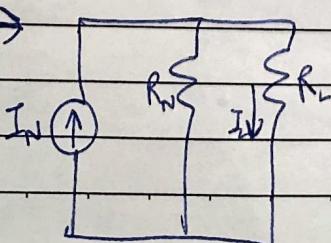

$$I_L = \frac{R_N}{R_N + R_L} \times I_N$$


Using KVL

$$12 - I_1 - 2I_1 - 3(I_1 + I_2) = 0 \Rightarrow 6I_1 + 3I_2 = 12 \Rightarrow 2I_1 + I_2 = 4$$

$$3(I_1 + I_2) - 2.5I_2 = 0 \Rightarrow I_2 = 1.5A$$

Page No.:


Date:

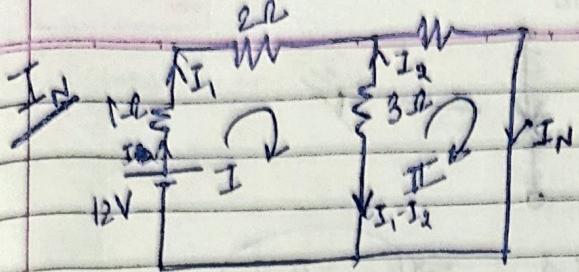

$$I_N = \frac{12}{1+2+\frac{2.5 \times 3}{2.5+3}} = \frac{12}{12} = 1A$$

$$I_N = \frac{12}{3+15} = \frac{12}{18} = \frac{2}{3}A$$

$$I_N = \frac{11}{4}A$$

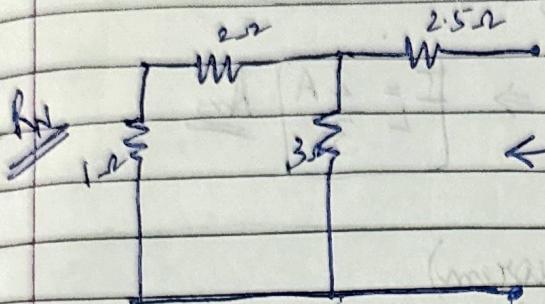


$$R_N = 2.5 + \frac{3 \times 3}{3+3} = 2.5 + 1.5 = 4\Omega$$

$$R_N = 2.5 + \frac{3 \times 2}{8.2} = 2.5 + \frac{3}{4} = 4\Omega$$


$$R_N = 4\Omega$$

$$I_L = \frac{R_N}{R_N + R_f} \times I_N = \frac{4}{4+5} \times \frac{12}{2} = \frac{4^2 \times 3}{9 \times 2} = \frac{6}{9}$$


$$I_L = \frac{2}{3}A$$

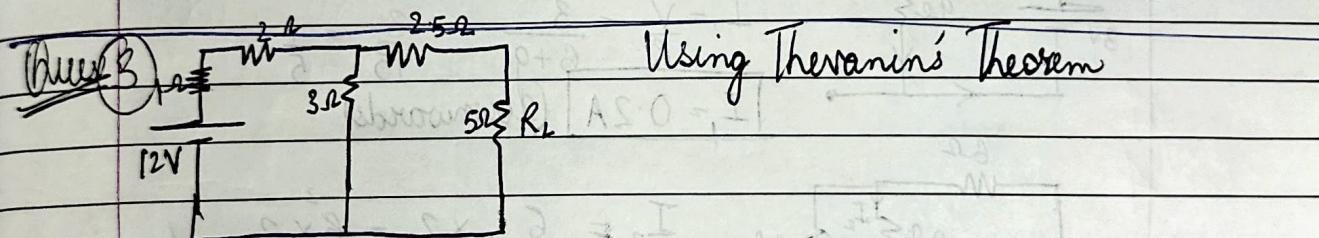

Using Thevenin's Theorem

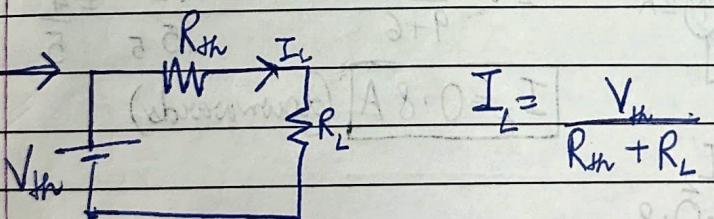

$$I_L = \frac{V_{Rth}}{R_{th} + R_L}$$

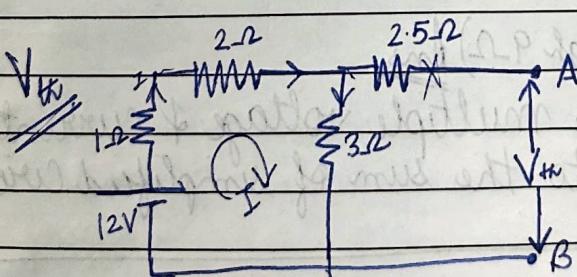


$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{1+2+3} = 2A$$

$$V_{Rth} = I \times 3\Omega = 2 \times 3V$$

$$V_{Rth} = 6V$$

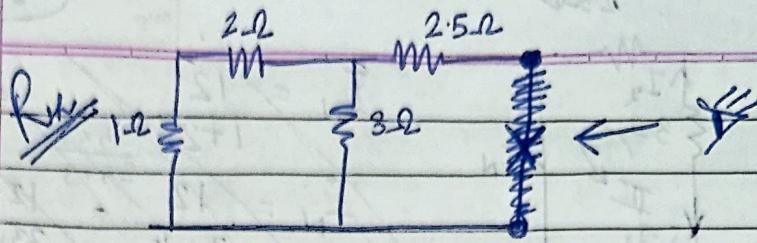


$$R_{th} = 2.5 + \frac{3 \times 3}{3+3} \Rightarrow R_{th} = 4 \Omega$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{6}{4+5} \Rightarrow I_L = \frac{2}{3} \text{ A} \quad \underline{\text{Ans}}$$

Q4. Using Superposition Theorem)

Find current through 9 ohm resistor

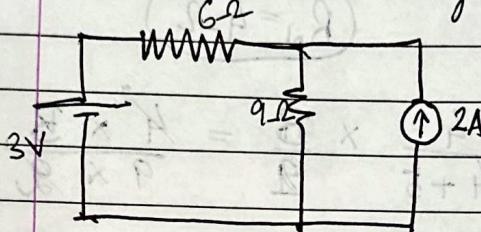

$$\rightarrow \begin{array}{l} \text{6 ohm resistor} \\ \text{9 ohm resistor} \\ \text{3V DC source} \end{array} \quad V = IR$$

$$I_1 = \frac{V}{R} = \frac{3}{6+9} = \frac{3}{15} = \frac{1}{5}$$

$$I_1 = 0.2 \text{ A} \quad (\text{downwards})$$

$$\begin{array}{l} \text{6 ohm resistor} \\ \text{9 ohm resistor} \\ \text{2A current source} \end{array} \quad I_2 = \frac{6}{9+6} \times 2 = \frac{6}{15} \times 2 = \frac{4}{5}$$

$$I_2 = 0.8 \text{ A} \quad (\text{downwards})$$


$$I = I_1 + I_2$$

$$I = 0.2 + 0.8$$


$$I = 1 \text{ A} \quad (\text{through 9 ohm}) \quad \underline{\text{Ans}}$$

In a circuit having multiple voltage & current sources is equal to the sum of simplified circu

Q③ (Using Superposition Theorem)

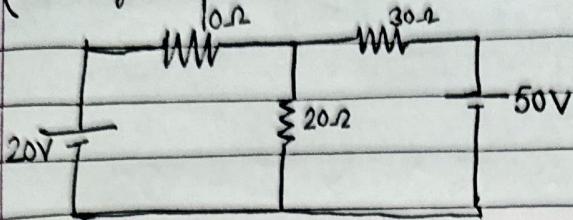

Find current through 20Ω Resistor

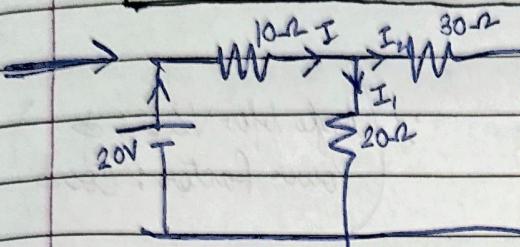


$$I = \frac{20}{10 + 20 + 30} = \frac{20}{60} = \frac{1}{3}$$

$$I = \frac{20}{10 + 20 + 30} = \frac{20}{60} = 0.9A$$

$$I_1 = \frac{30}{30 + 20} \times 0.9$$

$$(+) I_1 = \frac{30}{50} \times \frac{9}{10} = \frac{27}{50}$$

$$I_1 = 0.54 A \text{ (downwards)}$$

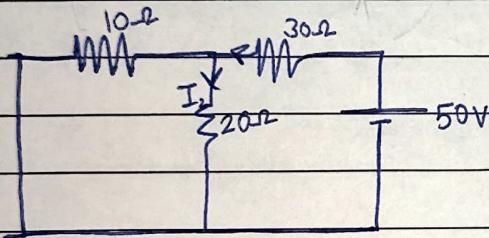

$$I = \frac{50}{30 + 20 + 10} = \frac{50}{60} = \frac{5}{6}$$

$$I_2 = \frac{10}{10 + 20} \times \frac{5}{6} = \frac{10}{30} \times \frac{5}{6} = \frac{5}{18} A$$

$$I_2 = 0.45 A \text{ (downwards)}$$

$$I = I_1 + I_2$$

$$I = 0.54 + 0.45$$


$$I = 1A \text{ (through } 20\Omega \text{)} \quad \text{Ans}$$

19/02/24

M	T	W	T	F	S	S
Page No.:						
Date:						

YOUVA

Power (AC Waveform)

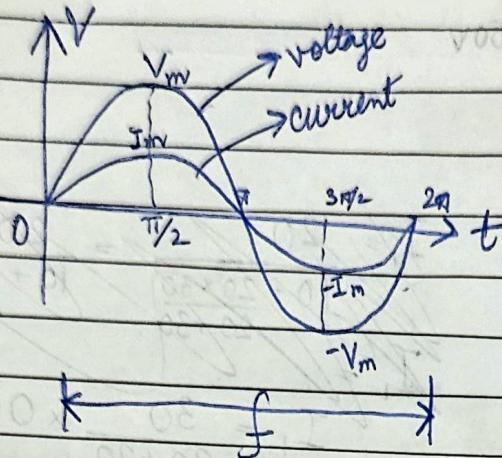

\therefore Angle b/w $V & I : \phi$
Power factor: $\cos \phi$

$$P(t) = V(t) \times I(t), \therefore P = VI \times \cos 0^\circ \quad (\text{in purely resistive circuit})$$


$$P = IRI$$

$$P = I^2 R *$$

$$P = \left(\frac{V}{R}\right)^2 R$$

$$P = \frac{V^2}{R} *$$

~~Do~~ ~~star~~ ~~star~~

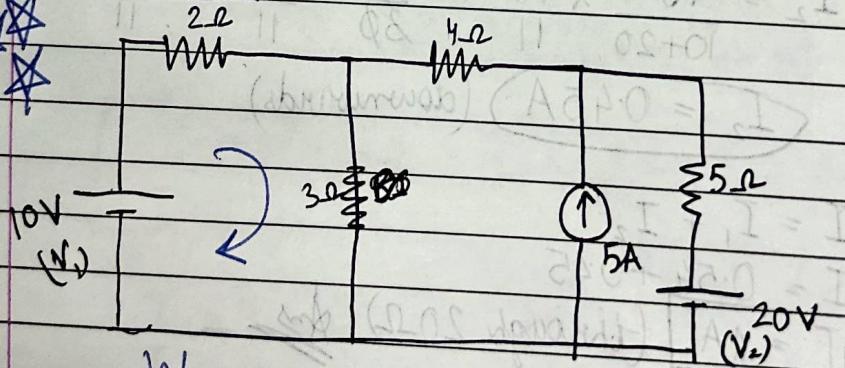

Using Superpos
Principle

$$\text{Ways: } I = I' + I'' + I'''$$

I' = Taking V_1 first shorting any other voltage source & opening current source


I'' = Taking V_2 then shorting V_1 & opening current source

I''' = Shorting all the voltage sources.

1/02/24

M	T	W	T	F	S	S
Page No.:	YOUVA					
Date:						

Power Triangle :-

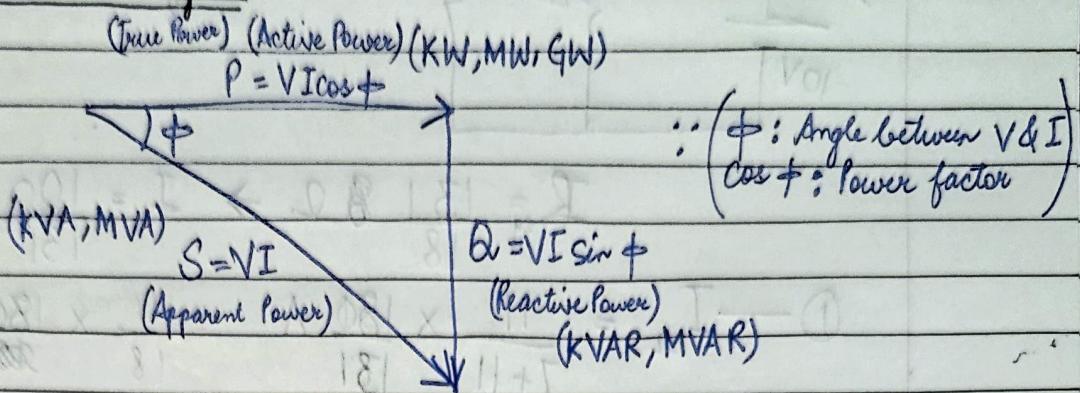

$$S^2 = P^2 + Q^2$$

- Load: Resistive Load where V & I are in same phase & P is always +ve
eg Electric Heater, Resistor, Light Lamp
- Inductive Load I lags V eg Transformer, Motor, Fan, Mobile Charger
- Capacitive Load I leads V eg
- ⇒ for single phase : (AC Circuit)
- ⇒ for three phase : (AC Circuit)

$$P = VI \cos \phi$$

$$P = \sqrt{3} VI \cos \phi$$


Instantaneous Power :- $P(t) = V(t) \times I(t)$

~~$$I = \frac{V}{Z}$$
 (impedance) and $Z = \sqrt{R^2 + (X_C - X_L)^2}$~~


~~$$X_L = 2\pi f L \quad \text{and} \quad X_C = \frac{1}{2\pi f C}$$~~

$$\bullet P = VI \cos \phi \quad (\text{Active Power})$$

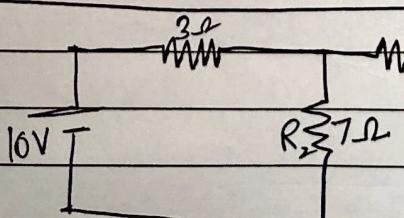⇒ $P \uparrow$ in order to compensate the decrease in ~~(cos φ)~~ value.




Find current through 7Ω.

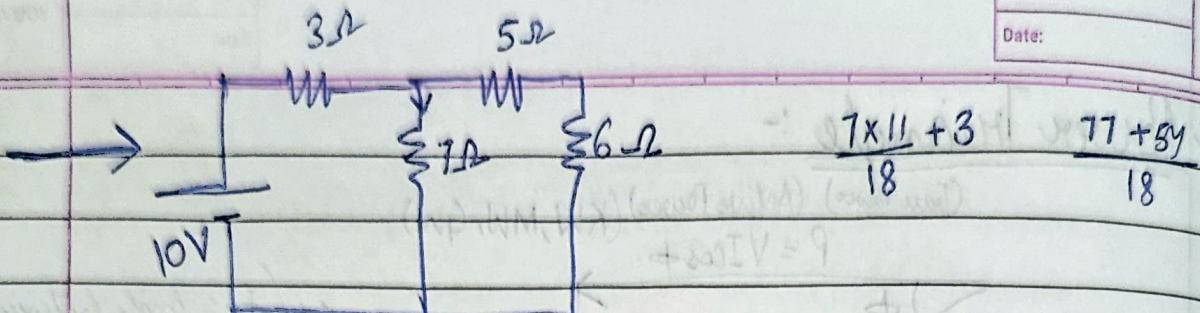

$$R_{eq} = \frac{131}{131} \Omega \Rightarrow I = \frac{100}{131} \text{ A}$$
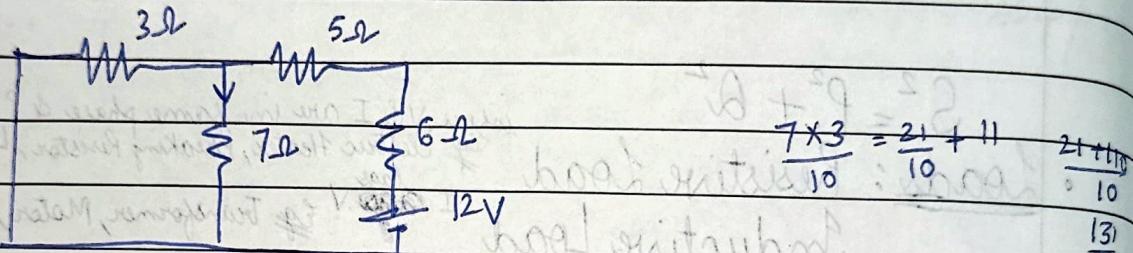
$$\textcircled{1} - I_{7\Omega} = \frac{11}{7+11} \times \frac{180}{18} \text{ A} = \frac{11}{18} \times \frac{180}{131} \text{ A} \text{ (downwards)}$$



$$R_{eq} = \frac{131}{10} \Omega \Rightarrow I = \frac{120}{131} \text{ A}$$

$$\textcircled{2} - I_{7\Omega} = \frac{3}{10} \times \frac{120}{131} \text{ A} \text{ (downwards)}$$

$\textcircled{1} + \textcircled{2} = \text{Total Current through } 7\Omega \text{ Resistor}$

